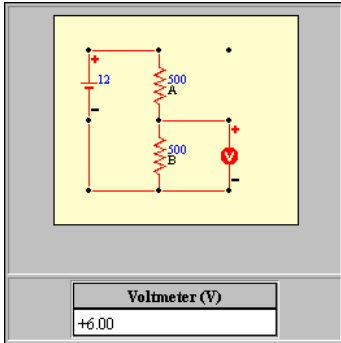


Worksheet for Exploration 30.3: Designing a Voltage Divider



Often with circuits, not only do you want to be able to figure out what a circuit that is already built is doing, you may want to design a circuit for a specific task. In this case, our task is to design a circuit that is a voltage divider with a particular output voltage (**voltage is given in volts and resistance is given in ohms**). You have a 12-V supply that can give you 1 W of power and you need a 4-V output with as much power as possible. The resistors that you have can dissipate 1 W of power.

To divide the voltage we can put the power supply in series with two resistors and then use the voltage across one of the resistors to be our 4-V output.

- a. What ratio of resistors do you need to divide the supply voltage by 1/3? In other words, how many times bigger (or smaller) should resistor A be than resistor B to get an output of 4 V? Try it.
 - i. Using $V = IR$, develop an expression for V as a function of R_A , R_B and the power supply voltage (12 V).
 - ii. For an output voltage of 4 V, what is the equation that relates R_A and R_B .
 - iii. Try it: $R_A = \underline{\hspace{2cm}}$ $R_B = \underline{\hspace{2cm}}$.
- b. Once the ratio is set up, do you have the maximum available power? To determine this, figure out the power used from the voltage source ($P = VI$). To get the maximum power (at a fixed voltage), should you increase or decrease the resistance in the circuit?

P from the power supply = .

- i. If you increase the total resistance in the circuit, will the power dissipated by the circuit increase or decrease? Explain.

c. What is the limit on the total resistance ($R_A + R_B$) and, therefore, the limit on each resistor. Try it.

i. What is the value of the current, I , for the maximum power from the power supply?

ii. What then, is the limit on the total resistance and the total resistance for each resistor?

d. Try using a smaller value of resistance. Does the power supply burn up? (Fortunately, you can simply restart the animation and try again).

e. Double the values of R_A and R_B . How much power does this circuit now draw from the battery?

Now that you have determined convenient values of R_A and R_B that produce a 4-Volt output, replace the voltmeter with a light bulb. (Adding a power consuming circuit element is sometimes referred to as adding a "load.")

f. When this light bulb is added, what is the voltage across the light bulb?

g. Why is it less than 4 V?

(Hint: Think about the current going through the light bulb.)

h. If you increase R_A and R_B more, what happens to the voltage across the light bulb? Why? This is the reason voltage dividers like this are made from resistors that are as small as possible.